

Name: Zhu Jin Shun

ID:22101071d

2421 A3 DL_Programming Experiment
Report

Requirement 1:The truth table in subtask two and the functions relating the output S_j and the input $E_0 E_1 E_2$.

Truth Table Subtask 2

Input			Output						
E_0	E_1	E_2	S_1	S_2	S_3	S_4	S_5	S_6	S_7
0	0	0	0	1	1	1	1	1	1
1	0	0	0	0	0	1	0	0	1
0	1	0	1	0	1	1	1	1	0
1	1	0	1	0	1	1	0	1	1
0	0	1	1	1	0	1	0	0	1
1	0	1	1	1	1	0	0	1	1
0	1	1	1	1	1	0	1	1	1
1	1	1	0	0	1	1	0	0	1

Function relating the output S_j and the input $E_0 E_1 E_2$.

$$S_1 = f(E_0 E_1 E_2) = E_0' E_1 E_2' + E_0 E_1 E_2' + E_0' E_1' E_2 + E_0 E_1' E_2 + E_0' E_1 E_2$$

$$S_2 = f(E_0 E_1 E_2) = E_0' E_1' E_2' + E_0' E_1' E_2 + E_0' E_1 E_2 + E_0 E_1' E_2$$

$$S_3 = f(E_0 E_1 E_2) = E_0' E_1' E_2' + E_0' E_1 E_2' + E_0 E_1 E_2' + E_0 E_1' E_2 + E_0' E_1 E_2 +$$

$$+E_0E_1E_2$$

$$= E_0E_2 + E_1 + E_0'E_2'$$

$$S_4=f(E_0E_1E_2)= E_0'E_1'E_2' + E_0E_1'E_2' + E_0'E_1E_2' + E_0E_1E_2' + E_0'E_1'E_2 + E_0E_1E_2$$

$$S_5=f(E_0E_1E_2)= E_0'E_1'E_2' + E_0'E_1E_2' + E_0'E_1E_2$$


$$S_6=f(E_0E_1E_2)= E_0'E_1'E_2' + E_0'E_1E_2' + E_0E_1E_2' + E_0E_1'E_2 + E_0'E_1E_2$$

$$S_7=f(E_0E_1E_2)= E_0'E_1'E_2' + E_0E_1'E_2' + E_0E_1E_2' + E_0'E_1'E_2 + E_0E_1'E_2 + E_0'E_1E_2 + E_0E_1E_2$$


$$= E_0+E_1'+ E_2$$

Requirement 2: Screen shot of the three circuits in three subtasks.


Subtask 1:

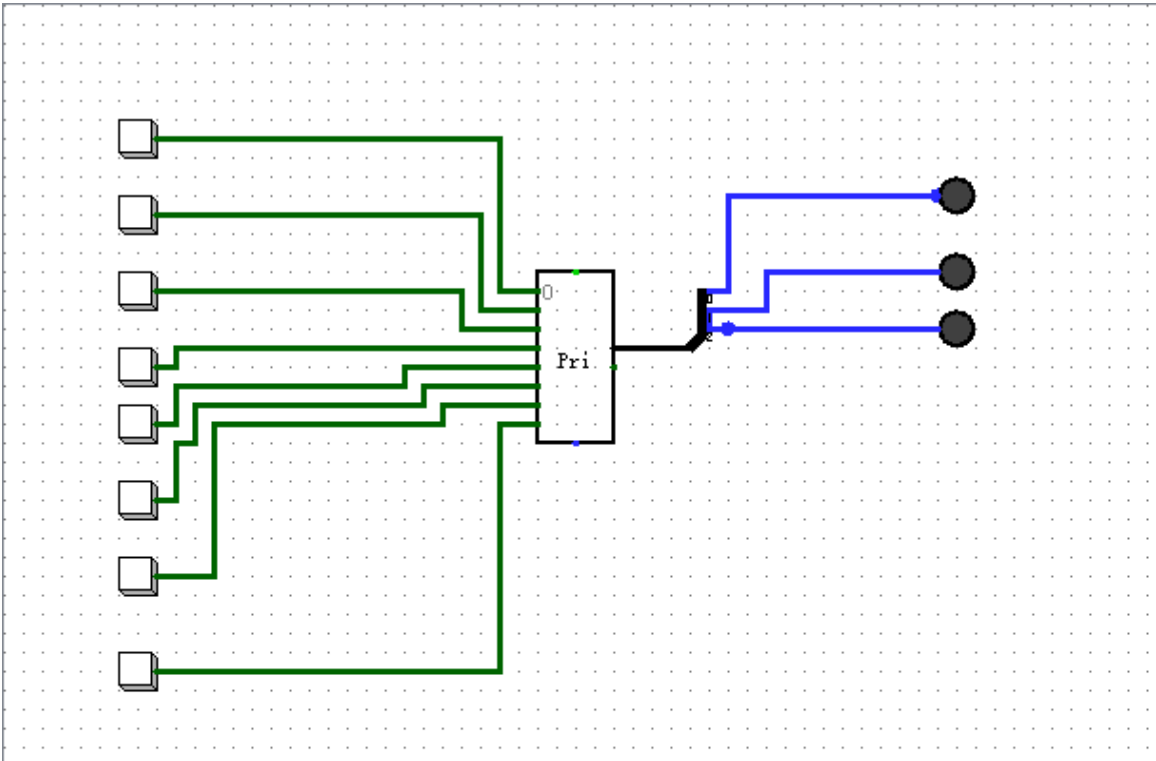

Subtask 2:

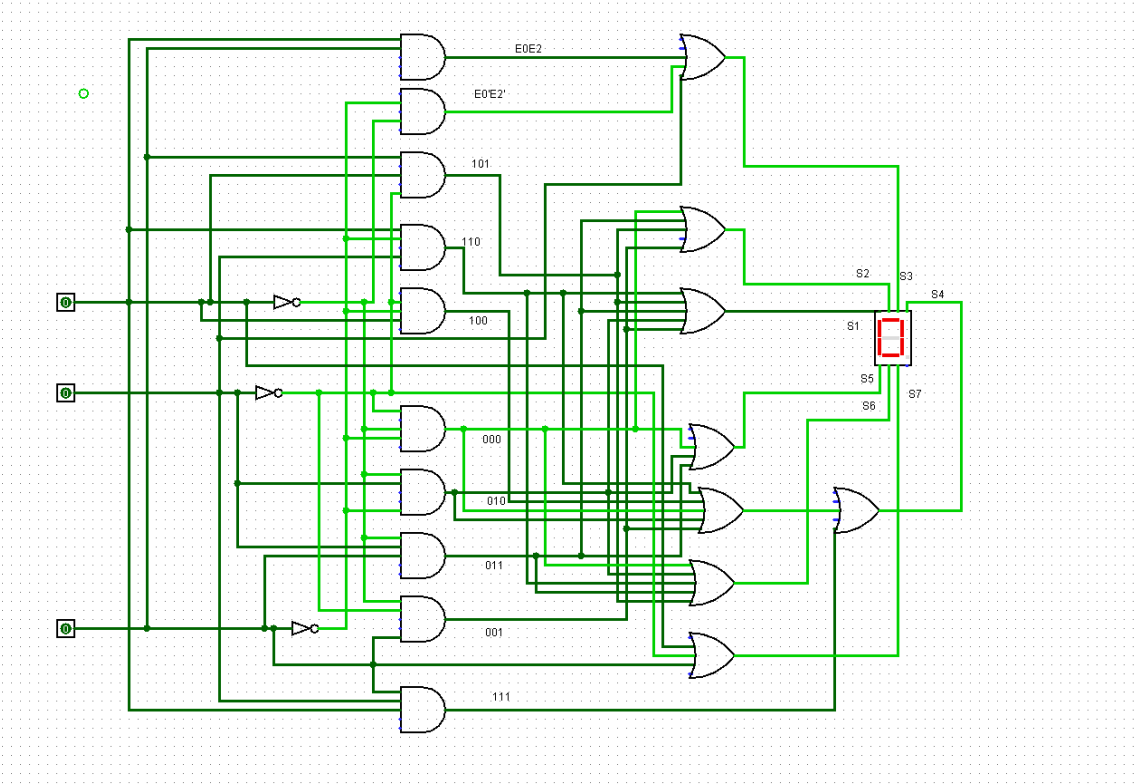


Subtask 3:

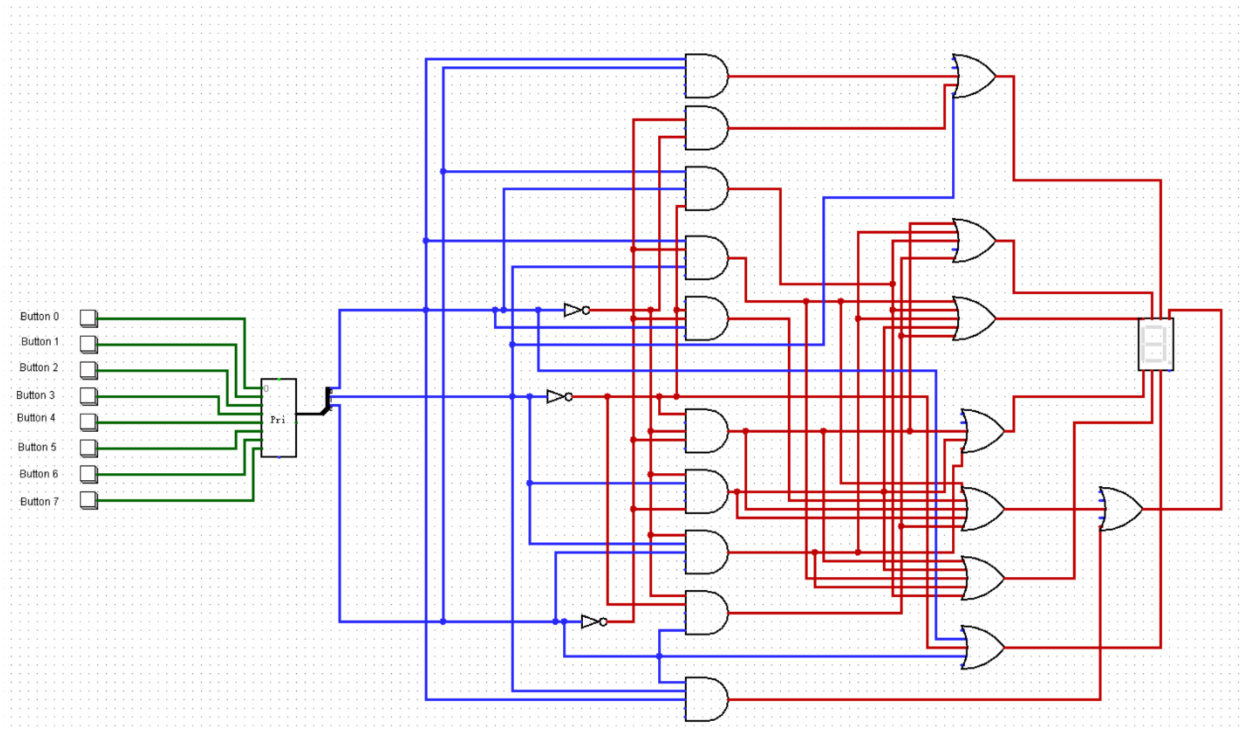


Requirement 3: Three pictures. In each picture, you should show that when button i is pressed, the digit i is shown in the 7-Segment display (Select three cases as you wish).

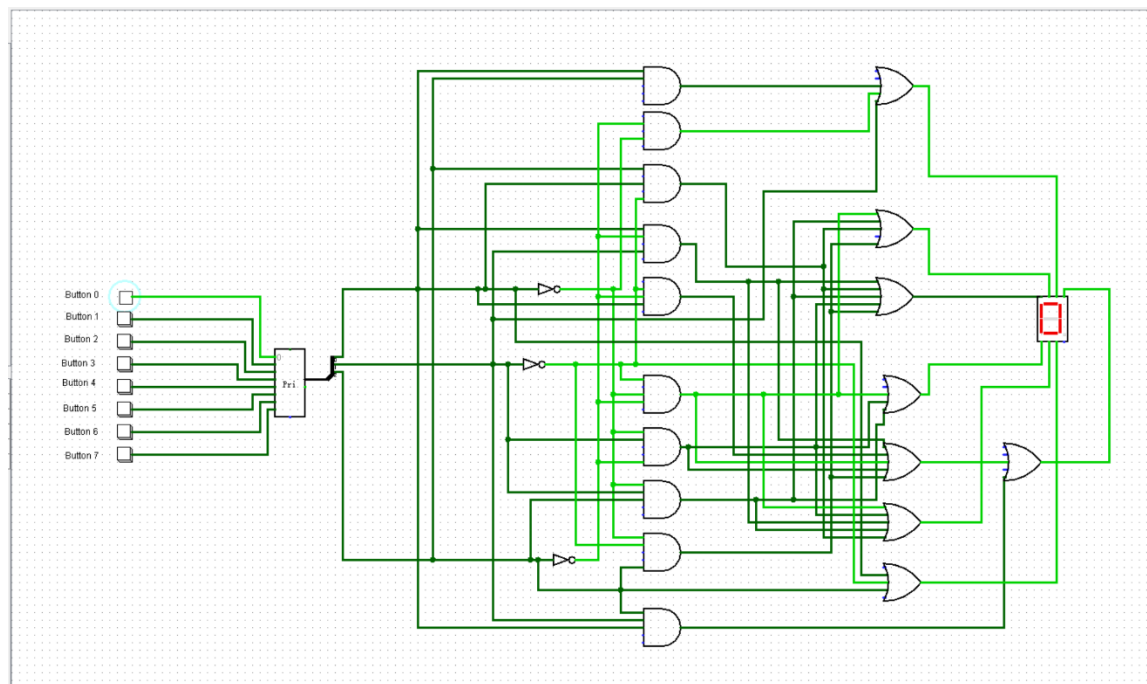When 0 is pressed, digit 0 is shown in 7-segment display:



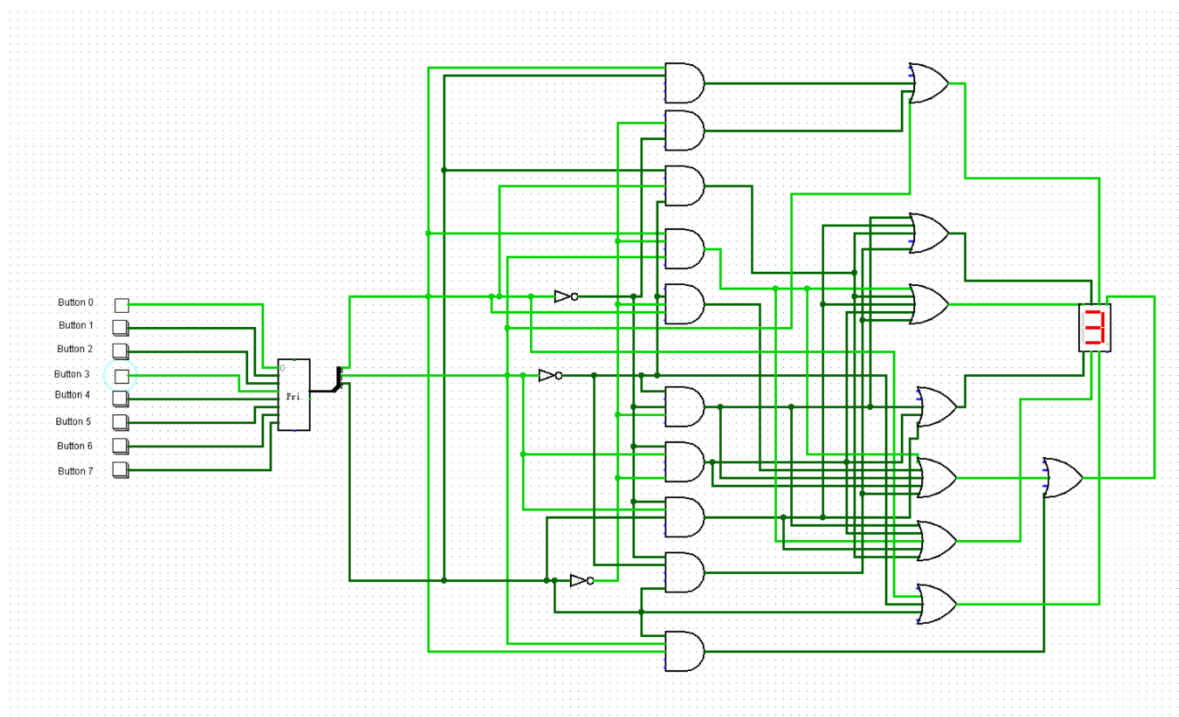When 3 is pressed, digit 3 is shown in 7-segment display:



When 6 is pressed, digit 6 is shown in 7-segment display:

